

Filtering of capacitors :

C parallel with load

[accept lowf , reject high f]

$$f = 0$$

$$X_C = \infty \quad Z = R \\ I = 0$$

$$f = \infty$$

$$X_C = 0 \quad Z \Rightarrow \text{it depends}$$

Filtering of inductors : $I = \text{max}$

L series with load

C accept low f , reject high f)

$$f < 0$$

$$f \geq (\text{high})$$

$$X_L < 0$$


$$X_L > (\text{high})$$

Low pass filter examples go

Low Pass Filter

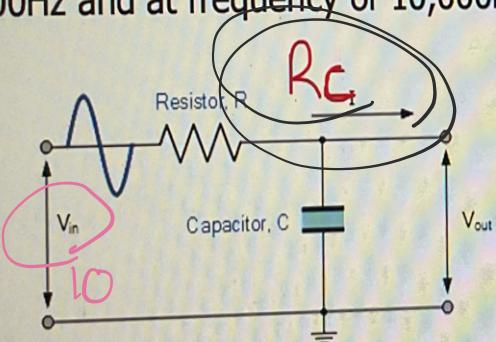Example:

A low pass filter circuit consisting of a resistor of $4.7\text{k}\Omega$ in series with a capacitor of 47nF is connected across a 10V sinusoidal supply. Calculate the output voltage (V_{OUT}) at a frequency of 100Hz and at frequency of $10,000\text{Hz}$ or 10kHz .



Voltage Output at a Frequency of 100Hz and 10kHz :

$$X_C = \frac{1}{2\pi f C}$$

$$V_{\text{OUT}} = V_{\text{IN}} \times \frac{X_C}{\sqrt{R^2 + X_C^2}}$$

$$f_1 = 100\text{Hz}$$

$$f_2 = 10,000\text{Hz}$$

$$R = 4.7\text{k}\Omega \text{ or } 4.7 \times 10^3 \Omega$$

$$\boxed{1} \quad X_C = \frac{1}{2\pi f C}$$

$$X_C = \frac{1}{6.28 \times 10,000 \times 47 \times 10^{-9}}$$

$$= \frac{1}{6.28 \times 100 \times 47 \times 10^{-9}}$$

$$= 338.8 \Omega$$

$$V = 10\text{V} \Rightarrow V_{\text{IN}}$$

$$= 33879.9 \Omega$$

$$V_{\text{output}} = ?$$

$$f_1 = 100\text{Hz}$$

$$f_2 = 10,000\text{Hz}$$

or
 10kHz

2

$$V_{\text{output}} \text{ for both } f_1 = 100\text{Hz}$$

$$\text{and } f_2 = 10,000\text{Hz}$$

$$V_{\text{out}} = V_{\text{in}} \frac{X_C}{\sqrt{R^2 + X_C^2}}$$

$$V_{\text{out}} = V_{\text{in}} \frac{X_C}{\sqrt{R^2 + X_C^2}}$$

$$= 10 \times \frac{33879.9}{\sqrt{(4.7 \times 10^3)^2 + (33879.9)^2}}$$

$$= 10 \times \frac{338.8}{\sqrt{(4.7 \times 10^3)^2 + (338.8)^2}}$$

$$= 9.9\text{V}$$

$$= 0.72\text{V}$$

extra

$$f_{\text{cutoff}} = ?$$

$$\boxed{35} \quad f_{\text{cutoff}} = \frac{1}{2\pi RC}$$


Because it's capacitor

$$= \frac{1}{6.28 \times 4.7 \times 10^3 \times 47 \times 10^{-9}}$$

$$= 720.8 \text{ Hz}$$

how to know if it is low or high pass check the circuit above?

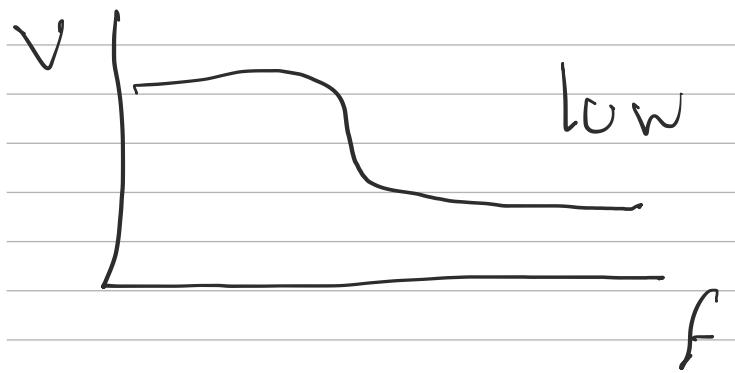if the capacitor parallel with load so it is low means accept low frequency and reject high frequency.




Filters

Low Pass Filter

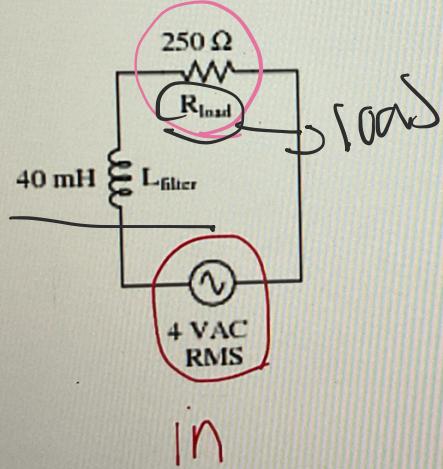Example:

$$R_L =$$

Identify the cut-off frequency of below circuit and calculate the output voltage at this frequency.



low pass

$$R = 250 \Omega$$

$$L = 40 \text{ mH}$$

$$\text{OR} \\ 40 \times 10^{-3} \text{ H}$$

$$V = 4 \text{ V} \Rightarrow \text{input } V_{in} \text{ in RMS}$$

$$\boxed{1} f_{\text{cutoff}} = \frac{R}{2\pi L}$$

$$= \frac{250}{6.28 \times 40 \times 10^{-3}}$$

$$\boxed{= 995.2 \text{ Hz}}$$

$$f_{\text{cutoff}} = ? ? \checkmark$$

$$\boxed{2} V_{out} = V_{in} \frac{R}{\sqrt{R^2 + X_L^2}}$$

$$V_{output} = ? ? \checkmark$$

$$\Rightarrow ??$$

$$R = X_L$$

$$X_L = 2\pi f L$$

$$= 6.28 \times 995.2 \times 40 \times 10^{-3}$$

$$\boxed{= 249.9 \Omega \approx 250 \Omega}$$

$$V_{out} = V_{in} \frac{R}{\sqrt{R^2 + X_L^2}}$$

$$250$$


$$4 \times \sqrt{2S_0^2 + \bar{S}_0^2}$$

$$= 2.8 \text{ V}$$

low pass

because the inductor

is in series with the load

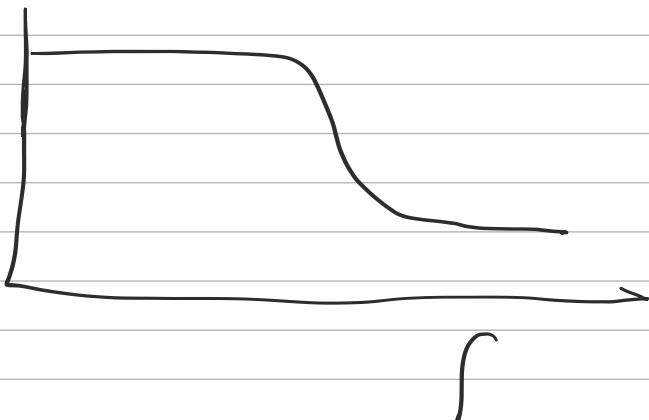


High pass filter examples:

High Pass Filter

$$V_{in} = 10$$

Example:

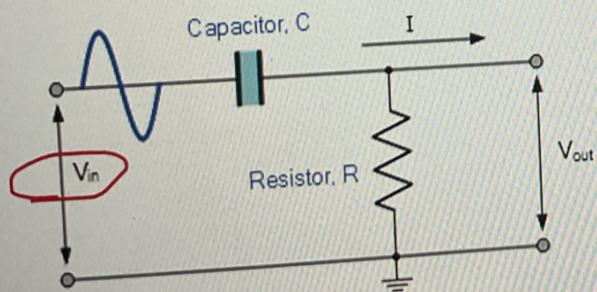- a) Calculate the cut-off or "breakpoint" frequency (f_c) for a simple passive high pass filter consisting of an 82pF capacitor connected in series with a 240kΩ resistor.



RC

$$f_{\text{cutoff}} = ?$$

$$f_{\text{cutoff}} = \frac{1}{2\pi RC}$$

$$C = 82 \text{ pF or}$$

$$82 \times 10^{-12} \text{ F}$$

$$R = 240 \text{ k}\Omega \text{ or } 240 \times 10^3 \Omega$$

$$= \frac{1}{6.28 \times 240 \times 10^3 \times 82 \times 10^{-12}}$$

$$= 8091.2 \text{ Hz}$$

$$V_{in} = 10$$

extra question
find V_{out} ??

$$V_{out} = V_{in} \cdot \frac{R}{\sqrt{R^2 + X_C^2}}$$

$$X_C = \frac{1}{2\pi F_C}$$

$$= \frac{1}{6.28 \times 8091.2 \times 82 \times 10^{-12}}$$


$$= 240001.3 \Omega$$

$$V_{out} = 10 \times \frac{240 \times 10^3}{\sqrt{(240 \times 10^3)^2 + (240001.3)^2}}$$

$$= 7.07 V$$

Example:

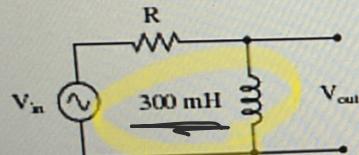(b) Identify what type of filter this circuit is, and calculate the size of resistor necessary to give it a cutoff frequency of 3 kHz:



R_L

$$R = ??$$

$$f_{cutoff} = \frac{R}{2\pi L}$$

$$f_{cutoff} = 3 \text{ kHz}$$

$$\text{or } 3 \times 10^3 \text{ Hz}$$

$$3 \times 10^3 = \frac{R}{6.28 \times 300 \times 10^{-3}}$$

$$L = 300 \text{ mH or}$$

$$300 \times 10^{-3} \text{ H}$$

$$(3 \times 10^3) \times (6.28 \times 300 \times 10^{-3}) = R$$

$$5652 = R$$

This is high pass filter
because the inductor is parallel
to the load.

Extra practices



AVT 2113 AC Electrical Fundamental Assignment
AC Filters Calculations
 Total Marks: 100

Name: Nouf Ahmed
 HCT's ID #: 100532259

The following electrical assignment covers calculating various values for alternating current circuits.

1. For the filter shown in the diagram, $V_{IN} = 10 \text{ V}$, identify the type of filter.
 Calculate the:

- (a) reactance of capacitor at 10 Hz, 1 kHz, and 100 kHz.
- (b) output voltage at each of these frequencies
- (c) cutoff frequency of the circuit
- (d) output voltage at cutoff frequency

$$V_{IN} = 10 \text{ V}$$

$$f_1 = 10 \text{ Hz}$$

$$f_2 = 1 \text{ kHz} \Rightarrow 1 \times 10^3$$

$$f_3 = 100 \text{ kHz} \Rightarrow 100 \times 10^3$$

$$f_{\text{cutoff}} = ??$$

$$V_{OUT} = ??$$

$$R = 1.8 \text{ k}\Omega \quad 1.8 \times 10^3$$

$$X_C = ??$$


$$C = 100 \text{ nF} \quad 100 \times 10^{-9}$$

D

$$f_{\text{cutoff}} = \frac{1}{2\pi RC}$$

$$= \frac{1}{2\pi \times 1.8 \times 10^3 \times 100 \times 10^{-9}}$$

$$= 884.6 \text{ Hz}$$

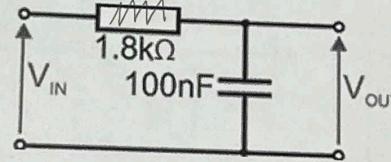

low

$$\boxed{D} \quad X_C = \frac{1}{6.28 \times 884.6 \times 100 \times 10^{-9}} \\ = 1800 \text{ }\mu\text{F}$$

$$\boxed{I} \quad V_{OUT} = 10 \times \frac{1.8 \times 10^3}{\sqrt{(1.8 \times 10^3)^2 + (1800)^2}} \\ = 7.07 \text{ V}$$

$$\boxed{II} \quad V_{OUT} = V_{IN} \frac{R}{\sqrt{R^2 + X_C^2}} \\ 10 \times \frac{1.8 \times 10^3}{\sqrt{(1.8 \times 10^3)^2 + (159235)^2}} \\ V_{OUT} = 0.11 \text{ V}$$

$$\boxed{I} \quad f_1 = 10 \text{ Hz}$$

$$X_C = \frac{1}{2\pi f C}$$

$$= \frac{1}{2\pi \times 10 \times 100 \times 10^{-9}} \\ = 159235.7 \text{ }\mu\text{F}$$

$$\boxed{II} \quad f_2 = 1 \times 10^3$$

$$X_C = \frac{1}{2\pi f C}$$

$$= \frac{1}{2\pi \times 1 \times 10^3 \times 100 \times 10^{-9}} \\ = 1592.4 \text{ }\mu\text{F}$$

$$\boxed{2} \quad V_{OUT} = V_{IN} \frac{R}{\sqrt{R^2 + X_C^2}}$$

$$10 \times \frac{1.8 \times 10^3}{\sqrt{(1.8 \times 10^3)^2 + (1592.4)^2}} \\ V_{OUT} = 7.48 \text{ V}$$

$$\boxed{3} \quad X_C = \frac{1}{2\pi \times 100 \times 10^3 \times 100 \times 10^{-9}} \\ = 15.9 \text{ }\mu\text{F}$$

$$f_3 = 100 \times 10^3$$

$$V_{OUT} = 10 \times \frac{1.8 \times 10^3}{\sqrt{(1.8 \times 10^3)^2 + (15.9)^2}} \\ V_{OUT} = 9.99 \text{ V}$$


2. Design and draw two high-pass filter circuits with a break frequency of 2kHz which uses a 22 nF capacitor and the other uses a 50mH inductor.

$$f = 2 \text{ kHz}$$


$$C = 22 \text{ nF}$$

$$L = 50 \text{ mH}$$

high

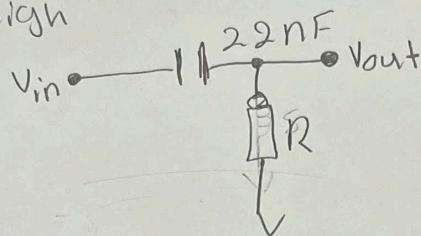

high

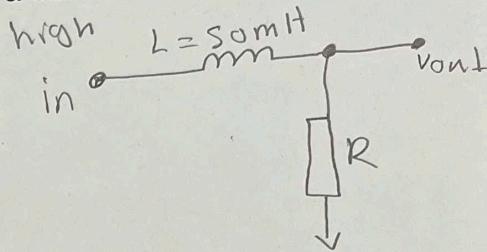

$$f_{\text{cutoff}} = \frac{1}{2\pi RC}$$

$$2 \times 10^3 = \frac{1}{6.28 \times R \times 22 \times 10^{-9}}$$

$$\boxed{R = 3590.3 \Omega}$$

$$f_{\text{cutoff}} = \frac{R}{2\pi L}$$


$$2 \times 10^3 = \frac{R}{6.28 \times 50 \times 10^{-3}}$$

$$\boxed{R = 628 \Omega}$$

3. Find the voltage gain of the filter circuit below,

$$f = 100 \text{ Hz}$$

high

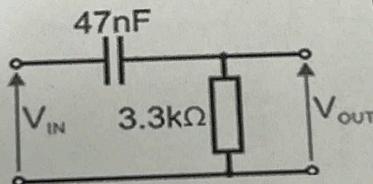

$$f = \frac{1}{2\pi RC}$$

$$C = 47 \times 10^{-9} \text{ F}$$

$$R = 3.3 \times 10^3 \Omega$$

$$V_{\text{in}} = ??$$

$$V_{\text{out}} = ??$$

$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{R}{\sqrt{R^2 + X_C^2}}$$

$$X_C = \frac{1}{6.28 \times 100 \times 47 \times 10^{-9}}$$

$$= 33879.9 \Omega$$

$$= \frac{3.3 \times 10^3}{\sqrt{(3.3 \times 10^3)^2 + (33879.9)^2}}$$

$$= 0.096$$