Resistive (R), Capacitive (C) and Inductive (L) circuits

Series AC Circuits

Impedance: may be illustrated by a right triangle.



 $Z^2 = R^2 + X_L^2$

The square root of both sides of the equation gives:

 $Z = \sqrt{R^2 + X_L^2}$

Resistance and reactance cannot be added directly, but they can be considered as two forces acting at right angles to each other

EX:



Figure 14-3. A circuit containing resistance and inductance.

 $X_L = 2 \pi \times f \times L$ The voltage drop across the resistance (ER) is: $X_{L} = 6.28 \times 60 \times 0.021$ $E^{R} = I \times R$ $X_L = 8$ ohms inductive reactance $Z = \sqrt{R^2 + X_L^2}$ $Z = \sqrt{\frac{6^2 + 8^2}{2}} = \sqrt{\frac{36 + 64}{4}}$

 $E^{R} = 11 \times 6 = 66$ volts The voltage drop across the inductance (E_{XL}) is:

 $E_{XL} = I \times X_L$ $E_{XL} = 11 \times 8 = 88$ volts

Then the current flow,

Z = 10 ohms impedance

 $I = \frac{E}{Z}$ $I = \frac{110}{10}$

 $Z = \sqrt{100}$

I = 11 amperes current

Ex:



$$\mathbf{X}_{\mathrm{L}} = 2\pi f \mathbf{L} = 2\pi \times 50 \times 0.5 = 157 \Omega$$

$$Z = \sqrt{R^{2} + X_{L}^{2}}$$

$$Z = \sqrt{30^{2} + 157^{2}}$$

$$Z = 159.8\Omega$$

$$V = 1.7 = 4 \times 159.8 = 640 \text{ w}$$

$$V_{\rm S} = 1.2 = 4 \times 159.8 = 640 \, {\rm v}$$

$$V_{R} = I.R = 4 \times 30 = 120v$$

$$V_{\rm L} = I.X_{\rm L} = 4 \times 157 = 628 v$$



Ex: Rc



Figure 14-4. A circuit containing resistance and capacitance.

$$200 \ \mu f = \frac{200}{1\ 000\ 000} = 0.000\ 200\ farads$$
$$X_{C} = \frac{1}{2\ \pi\ f\ C}$$
$$X_{C} = \frac{1}{6.28 \times 60 \times 0.002\ 00\ farads}$$
$$X_{C} = \frac{1}{0.075\ 36}$$
$$X_{C} = 13\ ohms\ capacitive\ reactance$$

To find the impedance:

$$Z = \sqrt{\frac{R^2 + X_c^2}{Z}}$$

$$Z = \sqrt{\frac{10^2 + 13^2}{100 + 169}}$$

$$Z = \sqrt{\frac{269}{Z}}$$

$$Z = 16.4 \text{ ohms capacitive reactance}$$

To find the current: $I = \frac{E}{Z}$ $I = \frac{110}{16.4}$

I = 6.7 amperes

Ex: RLC

$$R = 12\Omega \qquad L = 0.15H \qquad C = 100uF$$

$$V_{R} \qquad V_{L} \qquad V_{c} \qquad V_{c} \qquad V_{c} \qquad V_{s} = 100V, 50Hz$$

$$X_{L} = 2\pi fL = 2\pi \times 50 \times 0.15 = 47.13\Omega$$

$$X_{C} = \frac{1}{2\pi fC} = \frac{1}{2\pi \times 50 \times 100 \times 10^{-6}} = 31.83\Omega$$

$$Z = \sqrt{R^{2} + (X_{L} - X_{C})^{2}}$$

$$Z = \sqrt{R^{2} + (X_{L} - X_{C})^{2}}$$

$$Z = \sqrt{12^{2} + (47.13 - 31.83)^{2}}$$

$$Z = \sqrt{144 + 234} = 19.4\Omega$$

$$I = \frac{V_{S}}{Z} = \frac{100}{19.4} = 5.14$$
Amps

Parallel AC Circuits





$$IL = \frac{v}{xL} \qquad IC = \frac{v}{xC}$$

$$IL = \frac{240}{53.54} = 4.48A \qquad IC = \frac{240}{16.58} = 14.4A \qquad IR = \frac{240}{1000} = 0.24A$$

$$I = \sqrt{IR^2 + (IL - IC)^2} \qquad I = \sqrt{(0.24)^2 + (4.48 - 14.4)^2} = 9.9A$$

$$z = \frac{V}{I} = \frac{240}{9.9} = 24.24\Omega$$

$$Z = \frac{1}{\sqrt{\left(\frac{1}{R}\right)^2 + \left(\frac{1}{X_c} - \frac{1}{X_c}\right)^2}} = \frac{1}{\sqrt{\left(\frac{1}{1000}\right)^2 + \left(\frac{1}{53.54} - \frac{1}{16.58}\right)^2}}$$

$$Z = \frac{1}{\sqrt{1.0 \times 10^5 + 1.734 \times 10^{-3}}} = \frac{1}{0.0417} = 24.0\Omega$$



Series Resonance Circuit

Resonance occurs in a series circuit when the supply frequency causes the voltages across L and C to be equal and opposite in phase.



Resonance occurs in a series circuit when the supply frequency causes the voltages across L and C to be equal and opposite in phase.

$$X_{L} = X_{C} \implies 2\pi f L = \frac{1}{2\pi f C}$$

$$f^{2} = \frac{1}{2\pi L \times 2\pi C} = \frac{1}{4\pi^{2} LC}$$

$$f = \sqrt{\frac{1}{4\pi^{2} LC}}$$

$$\therefore f_{r} = \frac{1}{2\pi \sqrt{LC}} (Hz) \text{ or } \omega_{r} = \frac{1}{\sqrt{LC}} (rads)$$



Resonant Frequency, fr

V = 9volts

$$f_{\rm r} = \frac{1}{2\pi\sqrt{\rm LC}} = \frac{1}{2\pi\sqrt{0.02 \times 2 \times 10^{-6}}} = 796 {\rm Hz}$$

Circuit Current at Resonance, ${\sf I}_{\sf m}$

$$I = \frac{V}{R} = \frac{9}{30} = 0.3A$$
 or 300mA

Inductive Reactance at Resonance, X_L

$$X_{L} = 2\pi f L = 2\pi \times 796 \times 0.02 = 100 \Omega$$

Voltages across the inductor and the capacitor, $V_{\text{L}},\,V_{\text{C}}$

$$\begin{array}{l} V_{\scriptscriptstyle L} \ = \ V_{\scriptscriptstyle C} \\ V_{\scriptscriptstyle L} \ = \ I \times X_{\scriptscriptstyle L} \ = \ 300 \text{mA} \times 100 \Omega \\ V_{\scriptscriptstyle L} \ = \ 30 \text{ volts} \end{array}$$

I did not calculate the XC because its resonance frequency.

Power in AC Circuits

true power: is the product of the volts and the amperes in the circuit.

True Power Defined

1, The power dissipated in the resistance of a circuit, or the power actually used in the circuit.

2, In an AC circuit, a voltmeter indicates the effective voltage and an ammeter indicates the effective current.

Apparent Power Defined

1, It is the product of effective voltage times the effective current, expressed in voltamperes.

Ex:

2, It must be multiplied by the power factor to obtain true power available.

Power in AC Circuits

the true power is less than the apparent power. When there is capacitance or inductance in the circuit, the current and voltage are not exactly in phase,

power factor

power factor: is The ratio of the true power to the apparent power and is usually expressed in <u>percent</u>.

 $Power \ Factor \ (PF) = \frac{100 \times Watts \ (True \ Power)}{Volts \times Amperes \ (Apparent \ Power)}$

P = true power $P = I^2 R$ $P = \frac{E^2}{R}$ Measured in units of **Watts**

Q = reactive power $Q = I^2 X$ $Q = \frac{E^2}{X}$

Measured in units of Volt-Amps-Reactive (VAR)

S = apparent power
$$S = I^2 Z$$
 $S = \frac{E^2}{Z}$ $S = IE$
Measured in units of Volt-Amps (VA)

$$pr = \sqrt{pa^2 - pt^2}$$

Phase angel: formulas

$$\tan^{-1}\frac{x}{R} \quad or \ \tan^{-1}\frac{VL - VC}{VR}$$
$$\cos^{-1}\frac{R}{Z} \quad or \quad \cos^{-1}\frac{VR}{VS}$$
$$\sin^{-1}\frac{X}{Z} \quad or \quad \sin^{-1}\frac{VL - VC}{VS}$$