


Series AC circuit:

if AC circuit consists of R only,

The value of impedance same as R

$$Z = R$$
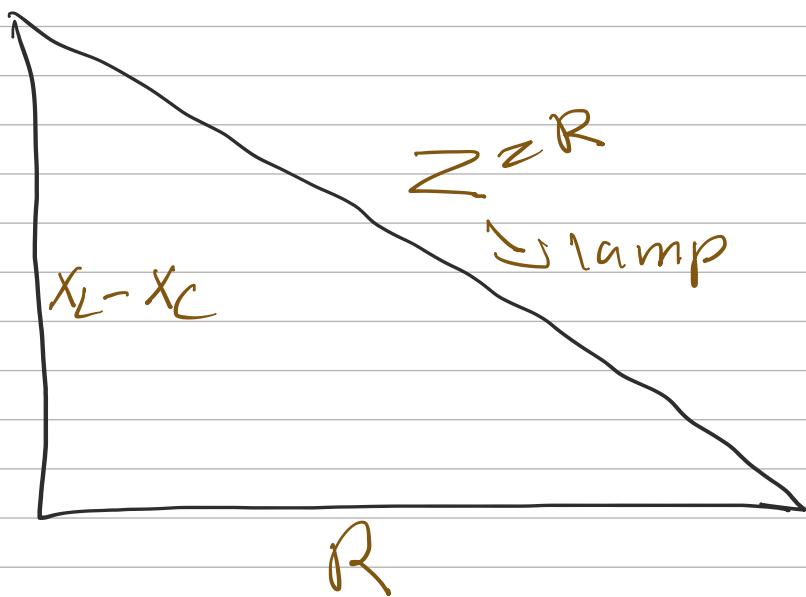
$$I = \frac{V}{Z} \Rightarrow \text{instant of } R$$



if AC consist of R and either $\{\text{L}\}$ or $\{\text{C}\}$,

The Z not same as R $Z \neq R$

$$Z^2 = R^2 + X_L^2$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

↓

دالة (رقم البير)
ناتج ارقم الفيفر
لهم

Examples :-

Resistive (R), Capacitive (C) and Inductive (L) Circuits

Resistors and Inductors (RL) in Series

Example: inductor

A series circuit consisting of 6Ω lamp and 0.021 H coil are connected in series to a source of 110 volts at 60 Hz. What is the value of the impedance and the current through the lamp and the coil?

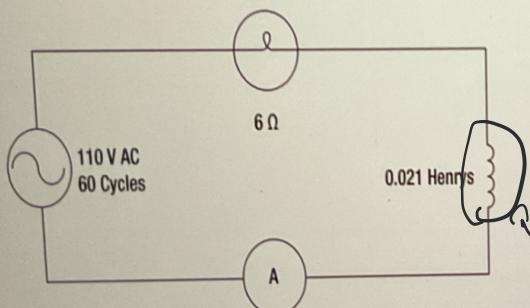


Figure 14-3. A circuit containing resistance and inductance.

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$X_C = \frac{1}{2\pi F C}$$

$$X_L = 2\pi F C$$

L coil is having X_L in its circuit

1) $R = 6\Omega$ lamp

$L = 0.021$ H coil

$V_s = 110$ V

$f = 60$ Hz

$Z = ?$?

$I = ?$?

2) $X_L = 2\pi F L$

$\therefore X_L = 6.28 \times 60 \times 0.021$

$= 7.9 \approx 8\Omega$

2) $Z = \sqrt{R^2 + X_L^2}$

unit (Ω) $= \sqrt{6^2 + 8^2}$

$$= 10 \Omega$$

[3] $I = \frac{V}{Z}$

unit
Ampere
(A)

$$= \frac{110}{10}$$

[I] = 11 A

Resistive (R), Capacitive (C) and Inductive (L) Circuits

Resistors and Capacitors (RC) in Series

Example: **Capacitor**

A series circuit in which a capacitor of $200 \mu F$ is connected in series with a 10Ω lamp. What is the value of the impedance, the current flow, and the voltage drop across the lamp?

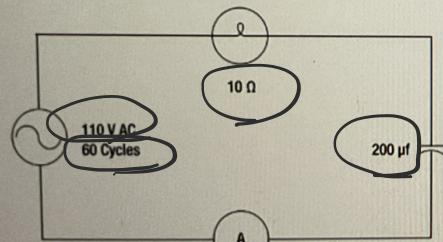


Figure 14-4. A circuit containing resistance and capacitance.

unit
 $\times 10^{-6}$ micro

$$C = 200 \mu F \text{ or } 200 \times 10^{-6} F$$

$$\Sigma X_C = \frac{1}{2\pi F C}$$

$$= \frac{1}{6.28 \times 60 \times 200 \times 10^{-6}}$$

= 13.3 \Omega

$$V = 110 V$$

$$Z = ??$$

$$I = ??$$

$$V_{drop} = ??$$

[2] $Z = \sqrt{R^2 + X_C^2}$

$$= \sqrt{10^2 + 13.3^2}$$

= 16.6 \approx 17 \Omega

$$[3] \quad I = \frac{V}{Z}$$

$$= \frac{110}{\sqrt{7}}$$

$$= 6.5 \approx 7A$$

$$[4] \quad V_{drop} = I \times R_{lamp}$$

↓
Total

$$= 6.5 \times 10$$

$$= 65V$$

Parallel AC Circuit:

$$\frac{1}{Z^2} = \frac{1}{R^2} + \frac{1}{X_L^2}$$

impedance

$$Z = \sqrt{\left(\frac{1}{R}\right)^2 + \left(\frac{1}{X_L} - \frac{1}{X_C}\right)^2}$$

Current :

$$I_R = \frac{V}{R}$$

Voltage :

$$V_R = IR$$

$$I_C = \frac{V}{X_C}$$

$$V_C = I \times X_C$$

$$I_L = \frac{V}{X_L}$$


$$V_L = I \times X_L$$

Resistive (R), Capacitive (C) and Inductive (L) Circuits

RCL Parallel Circuit

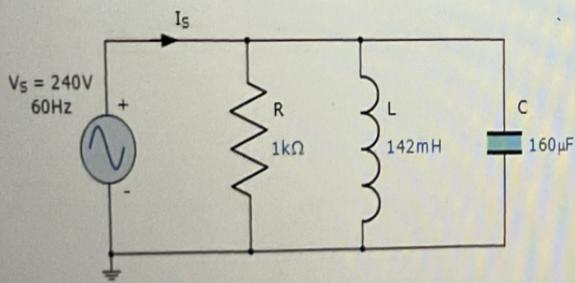Example:

A $1\text{k}\Omega$ resistor, a 142mH coil and a $160\mu\text{F}$ capacitor are all connected in parallel across a 240V , 60Hz supply. Calculate the impedance of the parallel RLC circuit and the current drawn from the supply.



$$R = 1 \text{ k}\Omega \text{ or } 1 \times 10^3 \Omega$$

$$L = 142 \text{ mH or } 142 \times 10^{-3} \text{ H}$$

$$C = 160 \mu\text{F} \text{ or } 160 \times 10^{-6} \text{ F}$$

$$V = 240 \text{ V}$$

$$f = 60 \text{ Hz}$$

$$Z = ? ?$$

$$I = ? ?$$

[Larger -] \rightarrow $\frac{1}{X_C}$
[Smaller.] \rightarrow $\frac{1}{X_L}$

$$\boxed{1} X_L = 2\pi f L \\ = 6.28 \times 60 \times 142 \times 10^{-3} \\ = 53.5 \Omega$$

$$X_C = \frac{1}{2\pi f C}$$

$$\frac{1}{6.28 \times 60 \times 160 \times 10^{-6}} \\ = 16.6 \Omega$$

$$\boxed{2} Z = \sqrt{\left(\frac{1}{R}\right)^2 + \left(\frac{1}{X_L} - \frac{1}{X_C}\right)^2}$$

$$= \sqrt{\left(\frac{1}{1 \times 10^3}\right)^2 + \left(\frac{1}{53.5} - \frac{1}{16.6}\right)^2} \\ = 24 \Omega$$

$$\boxed{3} I = \frac{V}{Z}$$


$$= \frac{240}{24}$$

$$= 10 \text{ A}$$

Resistive (R), Capacitive (C) and Inductive (L) Circuits RCL Parallel Circuit

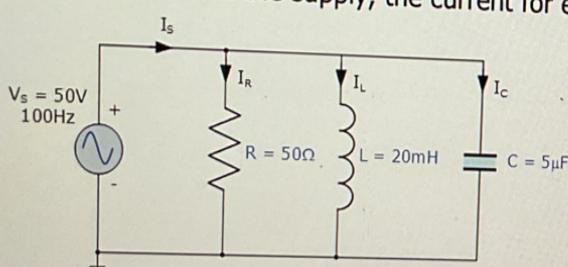Example:

A 50Ω resistor, a 20mH coil and a $5\mu\text{F}$ capacitor are all connected in parallel across a $50\text{V}, 100\text{Hz}$ supply. Calculate the total current drawn from the supply, the current for each branch, the total impedance of the circuit.



$$R = 50 \Omega$$

$$L = 20 \text{ mH or } 20 \times 10^{-3} \text{ H}$$

$$C = 5 \mu\text{F or } 5 \times 10^{-6} \text{ F}$$

$$V = 50 \text{ V}$$

$$f = 100 \text{ Hz}$$

$$I_C = ??$$

find current of
each branch

[1]

$$X_L = 2\pi f L$$

$$= 6.28 \times 100 \times$$

$$20 \times 10^{-3}$$

$$= 12.56 \Omega$$

$$X_C = \frac{1}{2\pi f C}$$

$$= \frac{1}{6.28 \times 100 \times 5 \times 10^{-6}}$$

$$= 318.5 \Omega$$

[2]

$$Z =$$

$$\sqrt{\left(\frac{1}{50}\right)^2 + \left(\frac{1}{318.5} - \frac{1}{12.56}\right)^2}$$

$$= 12.7 \Omega$$

$$I_R = ??$$

$$I_L = ??$$

$$I_C = ??$$

$$Z_T = ??$$

[3] $I_C = \frac{V}{Z_T}$

$$= \frac{50}{12.7}$$

$$= 3.9 \approx 4 \text{ A}$$

[4] $I_R = \frac{V}{R}$

$$I_L = \frac{V}{X_L}$$

$$= \frac{50}{50} = \frac{50}{12.56}$$

$$\boxed{I_R = 1 \text{ A}}$$

$$\boxed{= 3.91 \text{ A}}$$

$$I_C = \frac{V}{X_C}$$

$$= \frac{50}{318.5}$$

$$\boxed{= 0.1 \text{ A}}$$

parallel Resonance :-

in parallel resonance the inductor reactance and

capacitor reactance are equal $X_L = X_C$

$$f = \frac{1}{2\pi \sqrt{LC}}$$

inductor capacitor



6.28

→ Circuit impedance Z is

maximum

→ Circuit current I is
minimum

Circuit current is minimum.

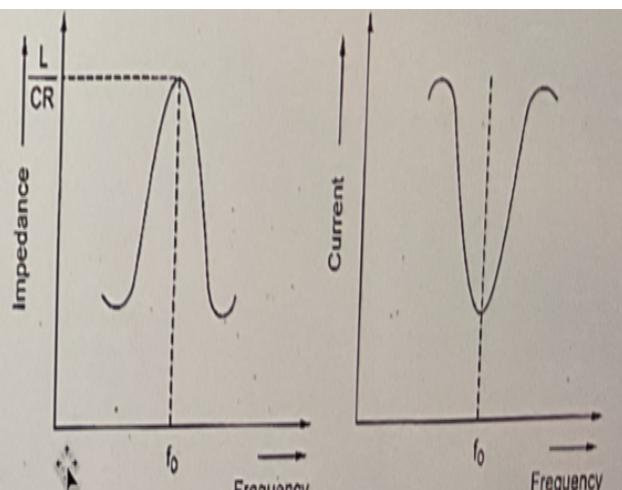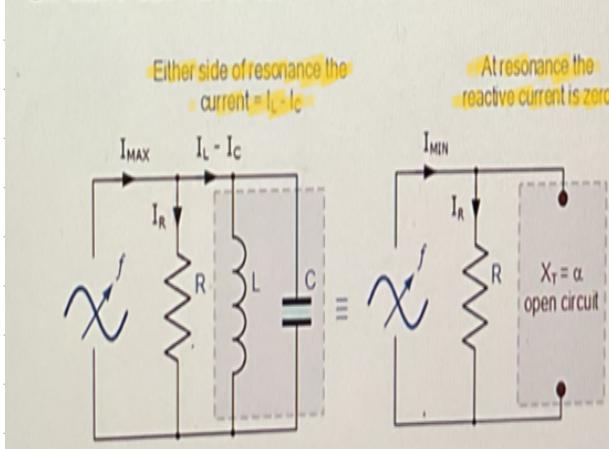


Parallel Resonance

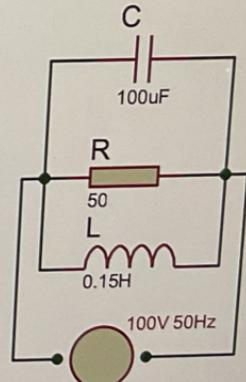Example:

A 50Ω resistor is placed in parallel with a 0.15H inductor and a $100\mu\text{F}$ capacitor with voltage supply of 100V , 50 Hz . Calculate:

- Resonant frequency
- The current in each branch
- The supply current
- The phase angle between supply current and supply voltage



$$R = 50\Omega$$

$$L = 0.15\text{H}$$

$$C = 100\mu\text{F} \text{ or } 100 \times 10^{-6}$$

$$V = 100\text{V}$$

$$f = 50\text{ Hz}$$

$$f_{\text{resonant}} = \frac{1}{2\pi\sqrt{LC}}$$

$$= \frac{1}{6.28 \times \sqrt{(0.15)(100 \times 10^{-6})}}$$

$$= 41.1 \text{ Hz}$$

$$f_{\text{resonant}} = ??$$

[2]

$$X_L = 2\pi f L$$

$$= 6.28 \times 50 \times$$

$$0.15$$

$$X_C = \frac{1}{2\pi f C}$$

$$\frac{1}{6.28 \times 50 \times 100 \times 10^{-6}}$$

$$= 31.8 \text{ mH}$$

I in each branch??

$$47.1 \text{ A}$$

$$[3] I_R = \frac{V}{R}$$

$$I_C = \frac{V}{X_C}$$

$$= \frac{10\phi}{5\phi}$$

$$= 2A$$

$$= \frac{100}{31.8}$$

$$= 3.1A$$

$$I_L = \frac{V}{Z_L}$$

$$= \frac{100}{47.1}$$

$$= 2.1A$$

$$\boxed{4} Z = \frac{1}{$$

$$\sqrt{\left(\frac{1}{50}\right)^2 + \left(\frac{1}{47.1} - \frac{1}{31.8}\right)^2}$$

$$= 44.5 \Omega$$

$$\boxed{5} I_T = \frac{V}{Z_T}$$

$$= \frac{100}{44.5}$$


$$= 2.2A$$

$\boxed{6}$ phase angle = ??

I_C


$\tan \theta = \frac{\text{opp}}{\text{adj}}$
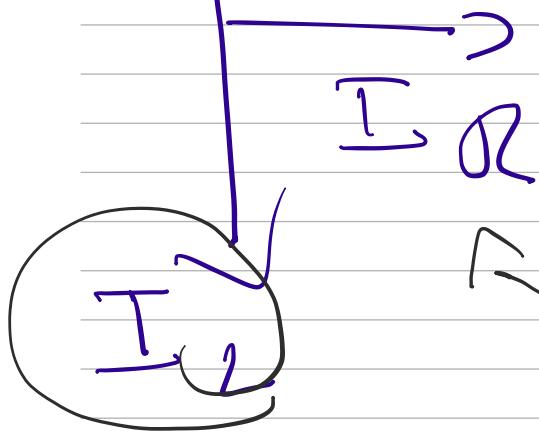
$$\theta = \tan^{-1} \left(\frac{1}{2} \right)$$



parallel مماثل


currents زوج

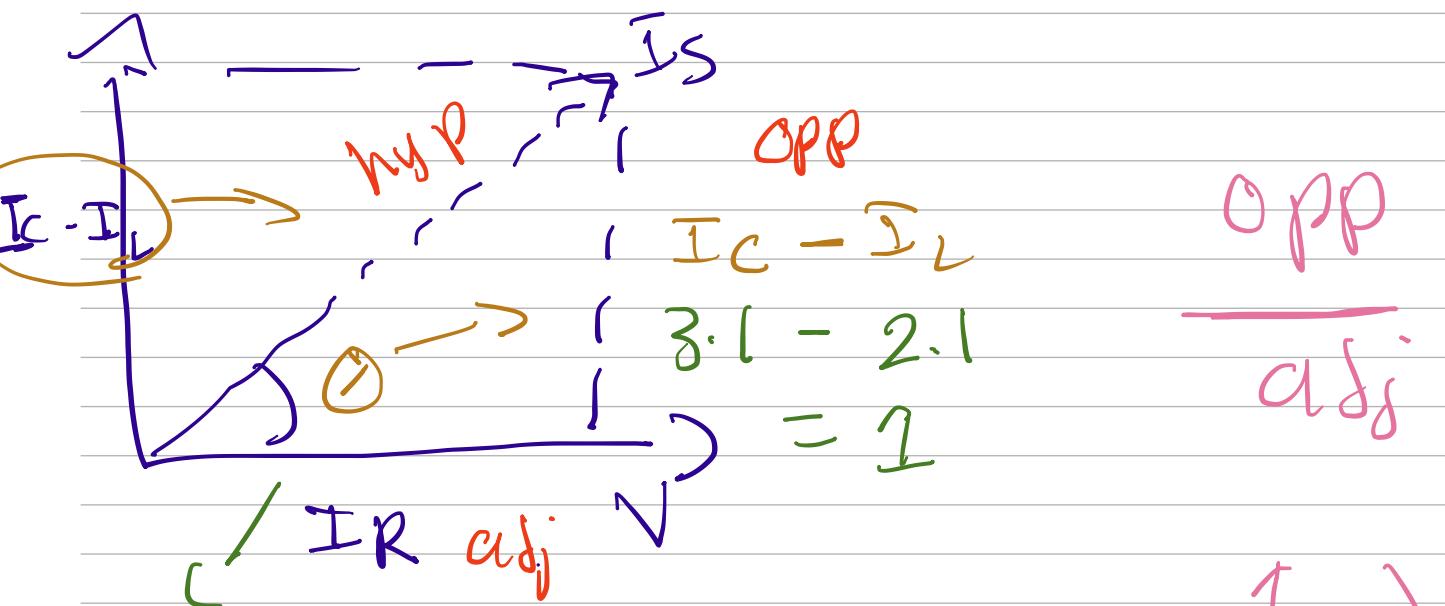

أرجواني الزاوية
opp > hyp angle
opp > adj

$$\tan^{-1} \left(\frac{1}{2} \right)$$

$$\theta = 26.56^\circ$$

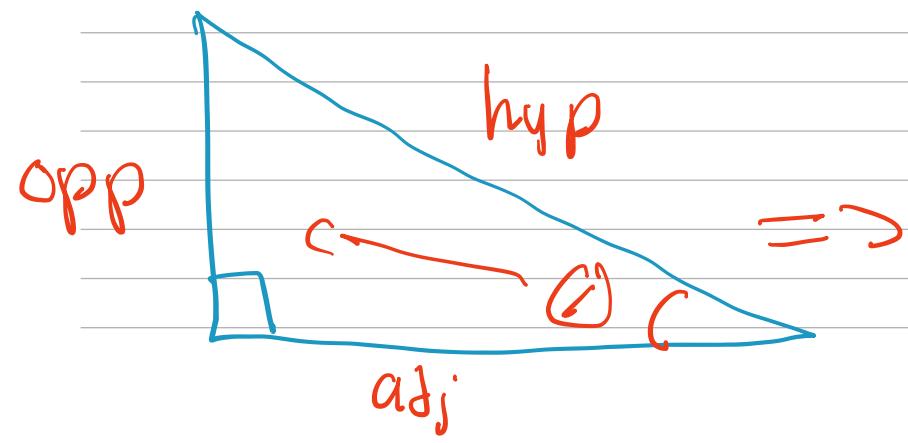

نستخرج من tan
لعلينا نفس الجواب جربوا

Series Resonance:

At series resonance the


inductor and capacitor is

$$\text{equal } X_C = X_L$$

→ circuit impedance Z
is minimum

→ circuit current I is
maximum.

$$f = \frac{1}{2\pi \sqrt{LC}}$$


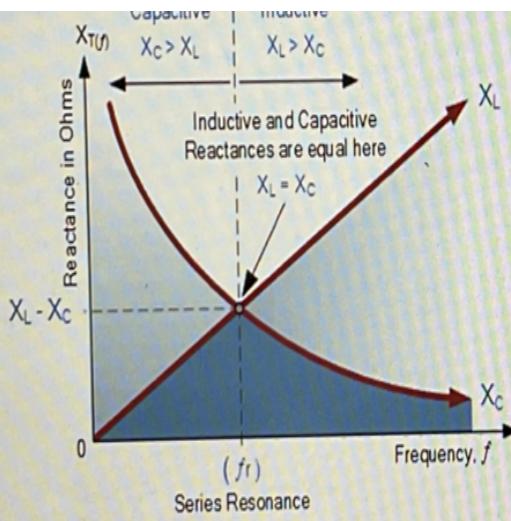


At series resonance:

- Circuit impedance is minimum
- Circuit current is maximum

Either side of resonance
the voltage drop = $V_L - V_C$

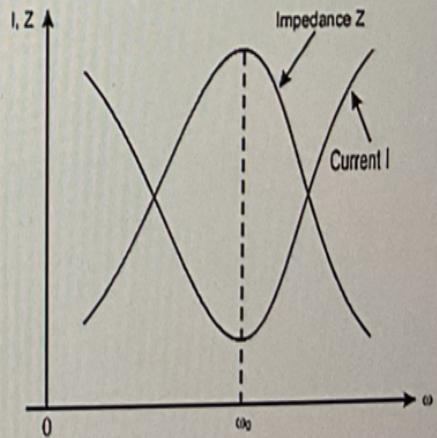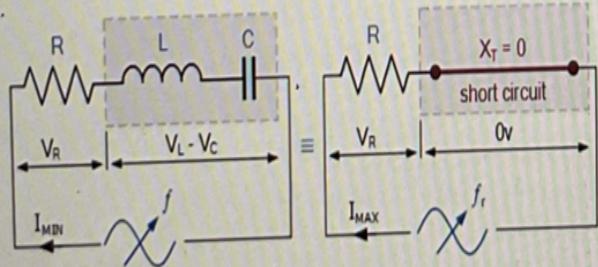At resonance the voltage drop equals zero




Series Resonance

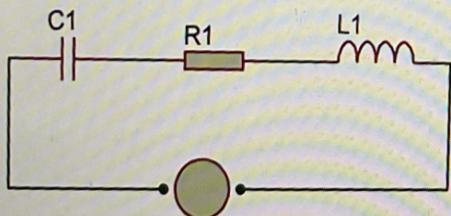Example:

In the following circuit at resonance, calculate: (1) The resonant frequency, (2) the current flowing in the circuit at resonance, (3) the voltage drop across each component at resonance.

[$C_1 = 60 \mu F$; $R_1 = 10 \Omega$; $L_1 = 125 mH$; Supply voltage = 120 V]



$$f_{resonant} = ? ? \checkmark$$

$$I_{at\ resonant} = ? ? \checkmark$$

$$\sqrt{\text{drop}} = ? ? \\ \text{across each component}$$

$$f_{resonant} = \frac{1}{2\pi \sqrt{LC}}$$

$$= \frac{1}{6.28 \times \sqrt{(125 \times 10^{-3}) \times (60 \times 10^{-6})}}$$

$$C_1 = 60 \text{ mF or } 60 \times 10^{-6} \text{ F}$$

$$= 58.14 \text{ Hz}$$

$$R_1 = 10 \Omega$$

$$L_1 = 12 \text{ s mH or } 12 \times 10^{-3} \text{ H}$$

$$V = 120 \text{ V}$$

$$\boxed{2} X_L = 2\pi f L \quad \left. \begin{aligned} X_C &= \frac{1}{2\pi f C} \\ &= \frac{1}{6.28 \times 58.14 \times 60 \times 10^{-6}} \\ &= 45.64 \Omega \end{aligned} \right\}$$

in series resonant the coil and capacitor are equal $X_L = X_C$

$$\boxed{3} Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$R = Z = \sqrt{10^2 + (45.64 - 45.64)^2} = 10 \Omega$$

$$\boxed{4} I_T = \frac{V}{Z} = \frac{120}{10} = 12 \text{ A}$$

$$\boxed{5} V_R = I R$$

$$= 12 \times 10$$

$$= 120 \text{ V}$$

$$V_C = I X_C$$

$$= 12 \times 45.64$$

$$= 547.68 \text{ V}$$

$$V_L = I X_L$$


$$= 12 \times 45.63$$

$$= 547.56 \text{ V}$$

Pure Resistor :-

$$R = \frac{V_{PK}}{I_{PK}}$$

$$R = \frac{V_{rms}}{I_{rms}}$$

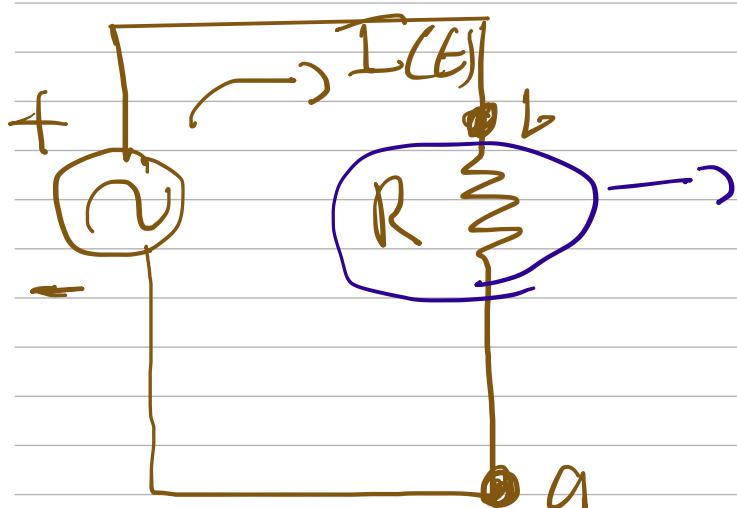

J.C.S.
resistor

unit Ohm (Ω)

Inductors in AC Circuits


unit ohm (Ω)

$$X_L = 2\pi f L$$

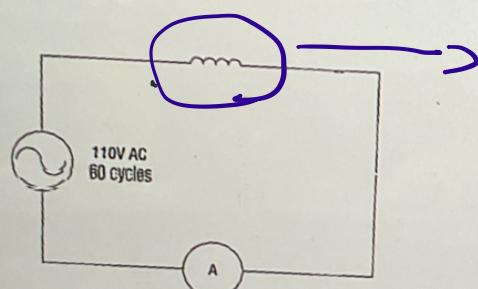6.28 constant

Inductors in AC circuits

- AC series circuit is shown in which the inductance is 0.146 Henry, and the voltage is 110 volts at a frequency of 60 cycles per second. Determine inductive reactance?



J.C.S.
inductor

$$L = 0.146 \text{ H}$$

$$X_L = 2\pi f L$$


$$v = 110 \text{ V}$$

$$f = 60 \text{ CPS}$$

$$= 6.28 \times 60 \times 0.146$$

$= 55.88$

$$X_L = ??$$

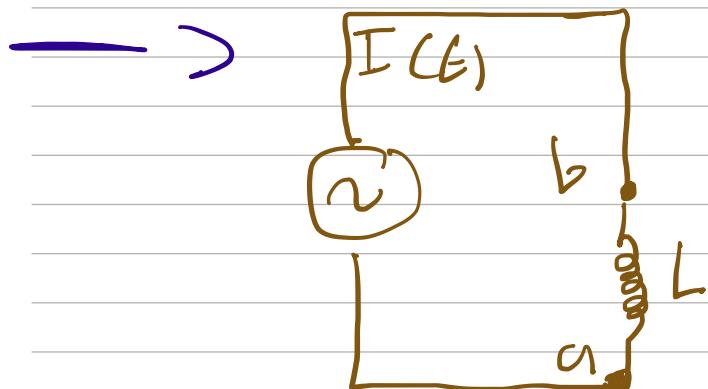

to find V_L :

$$V_L = I_L X_L$$

to find X_L

$$X_L = \frac{V_L}{I_L}$$

* Voltage across

pure inductor will

lead current by 90°

to find

$$I_L = \frac{V_L}{X_L}$$

$L \Rightarrow$ unit Henry (H)

Capacitor in AC circuits:

$$X_C = \frac{1}{2\pi F C}$$


unit Farad (F)

unit ohm (Ω)

Capacitive Reactance

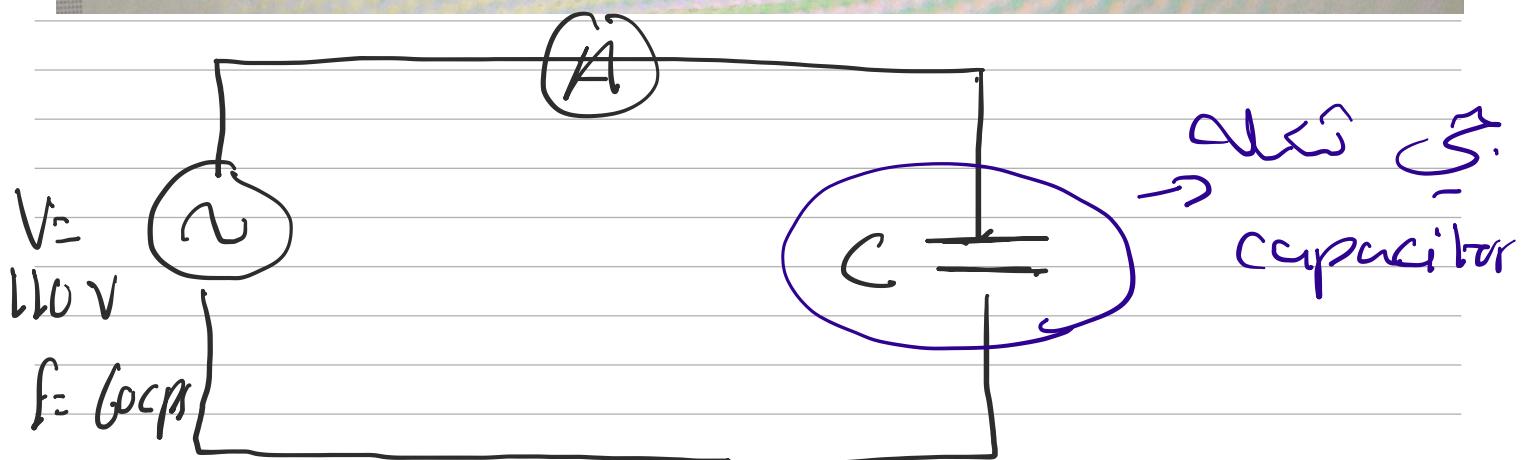Problem:

A series circuit is assumed in which the impressed voltage is 110 volts at 60 cps, and the capacitance of a condenser is $80 \mu\text{F}$. Find the capacitive reactance and the current flow.



$$V = 110 \text{ V}$$

$$f = 60 \text{ cps}$$

$$V = 110 \text{ V}$$

$$f = 60 \text{ cps}$$

$$C = 80 \mu\text{F}$$

or

$$80 \times 10^{-6} \text{ F}$$

$$X_C = \frac{1}{2\pi f C}$$

$$= \frac{1}{2 \times 3.14 \times 60 \times 80 \times 10^{-6}}$$


$$X_C = ??$$

$$= 33.17 \text{ } \Omega$$

→ Voltage containing pure capacitor will have large current

by 90° .

to find V :

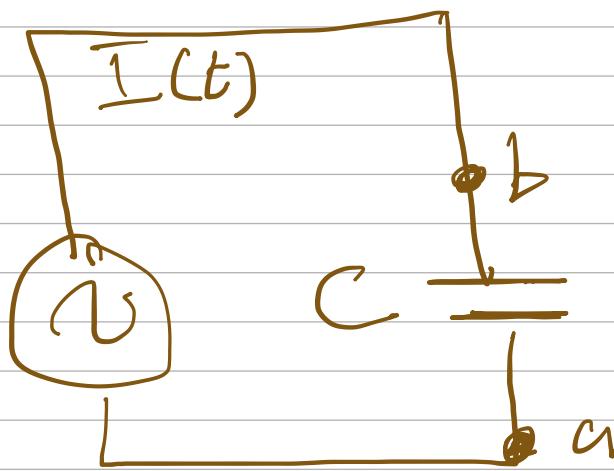

$$V_C = I \times X_C$$


to find X_C :

$$X_C = \frac{V_C}{I}$$

to find I_C :

$$I_C = \frac{V_C}{X_C}$$

phasor diagrams:

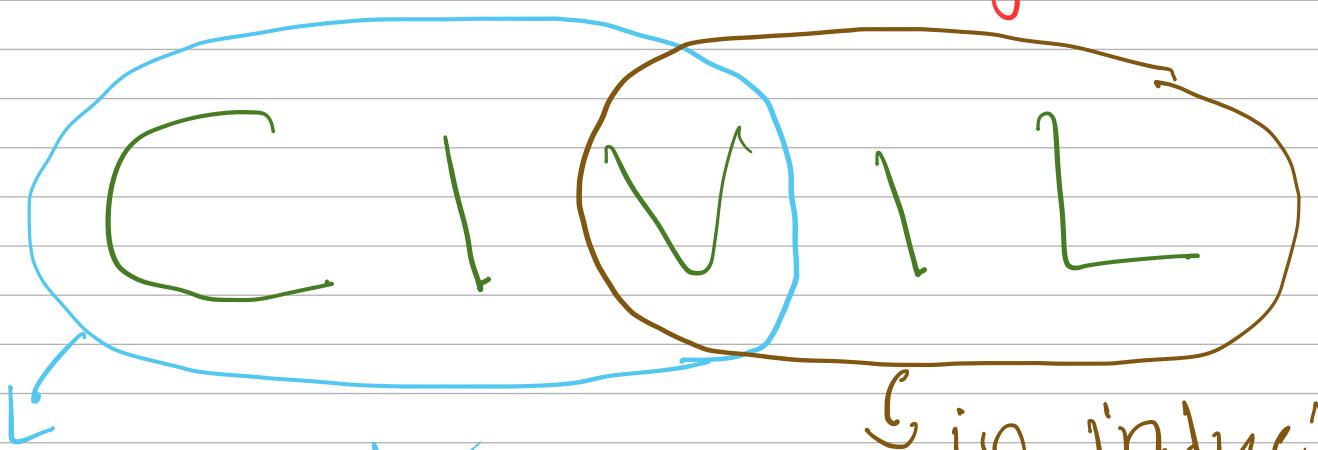

in capacitor

in inductor,
current lag

Current lead voltage.

Voltage


Resistors and Inductors (RL) in Series

Example:

RL Circuit

A coil has a resistance of 30Ω and an inductance of $0.5H$. If the current flowing through the coil is 4amps.

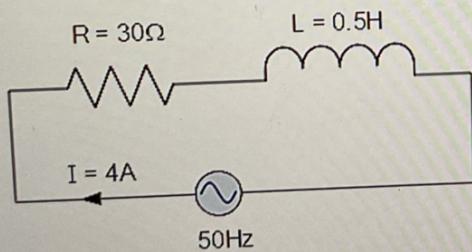- What will be the value of the supply voltage if its frequency is 50Hz?
- What will be the phase angle between the current and supply voltage?



$$X_L = 2\pi f L \quad I = \frac{V}{Z}$$

$$Z = \sqrt{R^2 + X_L^2} \quad \tan^{-1}\phi = \frac{X_L}{R}$$

1] $X_L = 2\pi f L$

$$= 6.28 \times 50 \times 0.5$$

$= 157 \Omega$

$$R = 30 \Omega$$

$$L = 0.5H$$

$$I = 4A$$

2] $Z = \sqrt{R^2 + X_L^2}$

$$= \sqrt{30^2 + 157^2}$$

$= 159.84 \Omega$

$$\theta = ??$$

between I and supply V

3] $I = \frac{V}{Z} \Rightarrow V = I Z$

$$= 4 \times 159.84$$

$= 639.36 V$

4] $\theta = \tan^{-1} \left(\frac{X_L}{R} \right)$

$$\tan^{-1} \left(\frac{157}{30} \right)$$


$= 79.18^\circ$

RLC Circuit

RLC Series Circuit

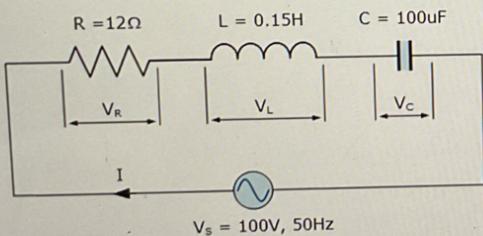Example:

A series RLC circuit containing a resistance of 12Ω , an inductance of $0.15H$ and a capacitor of $100\mu F$ are connected in series across a $100V$, $50Hz$ supply. Calculate the total circuit impedance and the circuit's current.



$$R = 12\Omega$$

$$\boxed{1} \quad X_C = \frac{1}{2\pi f C}$$

$$= \frac{1}{6.28 \times 50 \times 100 \times 10^{-6}}$$

$$= 31.88 \Omega$$

$$X_L = 2\pi f L$$

$$= 6.28 \times 50 \times 0.15$$

$$= 47.1 \Omega$$

$$V = 100V$$

$$\boxed{2} \quad Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$= \sqrt{12^2 + (47.1 - 31.88)^2}$$

$$= 19.4 \Omega$$

$$f = 50Hz$$

$$Z_T = ??$$

$$I_G = ??$$

$$\boxed{3} \quad I = \frac{V}{Z}$$

$$= \frac{100}{19.4}$$

$$= 5.15A$$

Power in AC circuit

Active power (P)
(Real power or True power)

$$P = I^2 R \quad P = \frac{V^2}{R}$$

obtained by "Wattmeter"
true using R circuit is its
power

Reactive power (Q)

$$Q = I^2 X \quad Q = \frac{V^2}{X}$$

\nwarrow Impedance

x_L and x_C

it measured in VAR


(Volt-ampere-reactive)

Reactive power is in X circuit lies in

Apparent power (S)

$$S = I^2 Z \quad S = \frac{V^2}{Z} \quad S = I V$$


measured in VA (volt-ampere)

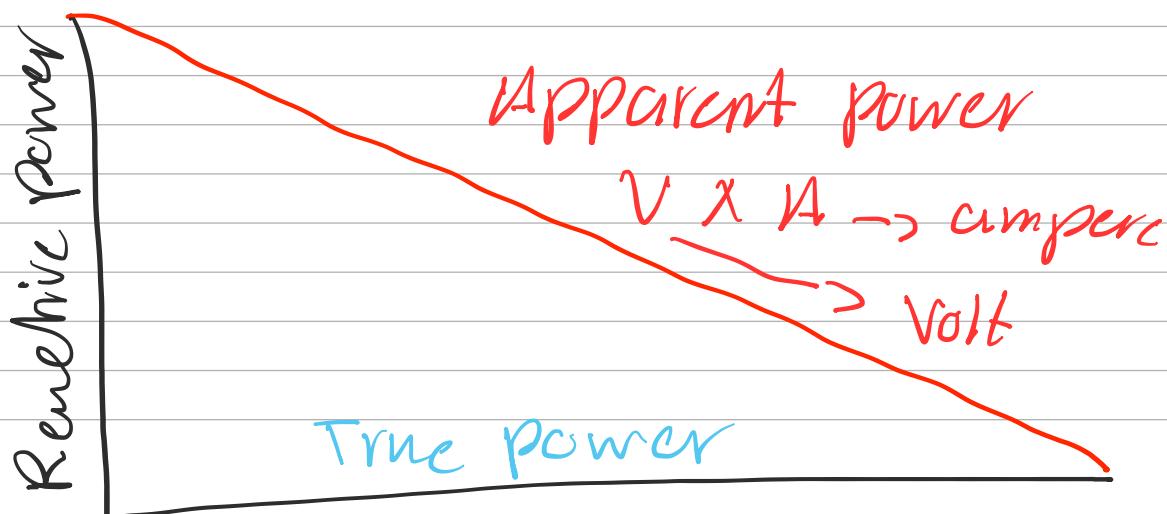

Example ☺

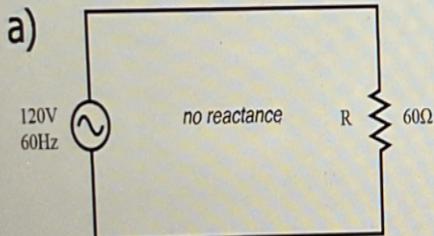Example:


Find the true power, reactive power and apparent power for below circuits:



True power

$$Q=0$$


$$P=V^2/R$$

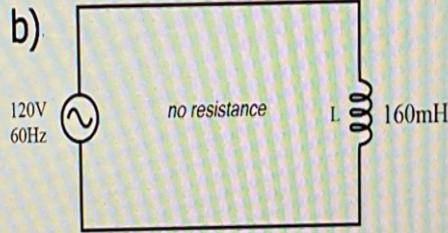

b) L lies and
Reactive power

II True power

$$R \text{ lies to } Q \rightarrow P=0$$

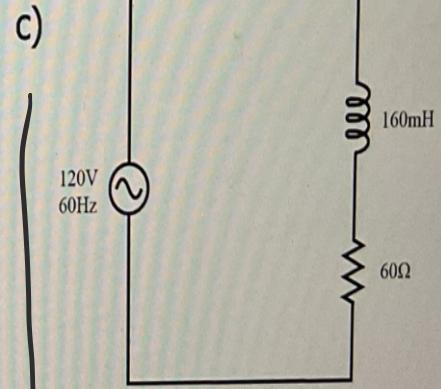

c) Circuit lies and
R and X

II True power

$$V=120 \quad P=I^2 R$$

$$f=60 \quad I=\frac{V}{R}=\frac{120}{60}$$

$$R=60 \quad I=2A$$

$$L=160 \times 10^{-3} \quad \boxed{I=2A}$$

R lies and
true power

II True power:

$$V=120V$$

$$f=60Hz$$

$$R=60\Omega$$

II Reactive power

$$X_L = 2\pi f L$$

$$= 6.28 \times 60 \times 160 \times 10^{-3}$$

$$\boxed{= 60.28 \Omega}$$

$$P=I^2 R$$

$$= 2^2 \times 60$$

$$\boxed{= 240 W}$$

2

II Reactive power

$$P = I^2 R$$

$$I = \frac{V}{R} = \frac{120}{60}$$

$$I = 2 \text{ A}$$

$$P = I^2 R$$

$$= 2^2 \times 60$$

$$= 240 \text{ W}$$

2) Reactive power

There is no reactive power.

So X is the reactive power.

True power = $S \rightarrow$ Apparent power

$$Q = \frac{V^2}{X} \rightarrow X_L$$

$$= \frac{120^2}{60 \cdot 28}$$

$$= 238.88 \text{ VAR}$$

3) Apparent power

P is the real part of the voltage Q is the imaginary part of P

$$S = Q$$

$$Q = \frac{V^2}{X}$$

$$X_L = 2\pi f L$$

$$= 6.28 \times 60 \times 160 \times 10^{-3}$$

$$= 60.28 \text{ mH}$$

$$Q = \frac{V^2}{X}$$

$$= \frac{120^2}{60 \cdot 28}$$

$$= 238.88 \text{ VAR}$$

3) Apparent power

$$S = \sqrt{P^2 + Q^2}$$

$$= \sqrt{240^2 + 238.88^2}$$

$$= 338.6 \text{ VA}$$

Power Factor

$P \rightarrow$ true power

$$PF = \frac{P}{S} \times 100$$

$S \rightarrow$ Apparent power

Power Factor

Example:

A 220-volt AC motor takes 50 amperes from the line, but a wattmeter in the line shows that only 9350 watts are taken by the motor. What are the apparent power and the power factor?

$$V = 220V$$

1)

$$I = 50A$$

$$S = IV$$

$$P = 9350W$$

↳ True power
(wattmeter)

$$= 50 \times 220$$

$$= 11000VA$$

$$S = ??$$

2)

Apparent
power

$$PF = \frac{P}{S} \times 100$$

$$PF = ??$$

$$= \frac{9350}{11000} \times 100$$

$$= 85\%$$

Useful Formulas:

$$\text{Capacitive Reactance: } X_C = \frac{1}{2\pi f C}$$

$$\text{True Power: } P = I^2 R$$

$$\text{Inductive Reactance: } X_L = 2\pi f L$$

$$\text{Reactive Power: } P_R = I^2 X$$

$$\text{Impedance (series): } Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\text{Apparent Power: } P_A = I^2 Z$$

$$\text{Impedance (parallel): } \frac{1}{Z} = \sqrt{\left(\frac{1}{R}\right)^2 + \left(\frac{1}{X_L} - \frac{1}{X_C}\right)^2}$$

$$\text{Cut-off Frequency: } f_C = \frac{1}{2\pi RC}$$

$$\text{Resonance Frequency: } f_R = \frac{1}{2\pi\sqrt{LC}}$$

Now fi AL bcdwnni