

Nouf
Albedwawi

C104. part 1.

Resistance / Resistor

Resistance of material

$$R = \frac{\rho \times L}{A}$$

$R \Rightarrow$ Resistor Ω

$\rho \Rightarrow$ Resistivity of material
in circular mil ohms
per foot

$L \Rightarrow$ its length in feet

$A \Rightarrow$ Area in circular mils

Resistor and wire sizes

$$\frac{R_1}{L_1} = \frac{R_2}{L_2} \times \frac{A_1}{A_2}$$

Example: A conductor that is 1 m long with cross section area of 1 mm², has R of 0.017 Ω , what is the resistance of 50 m of wire from the same material but with cross section area of 0.25 mm²?

①

$$\begin{aligned} L_1 &= 1 \text{ m} \\ R_1 &= 0.017 \Omega \\ A_1 &= 1 \text{ mm}^2 \end{aligned}$$

②

$$\begin{aligned} R_2 &= ?? \\ L_2 &= 50 \text{ m} \end{aligned}$$

③

$$\frac{R_1 A_1}{L_1} = \frac{R_2 A_2}{L_2}$$

$$A_2 = 0.25 \text{ mm}^2$$

$$\frac{R_1}{L_1} \cdot A_1 = \frac{R_2}{L_2} \cdot A_2$$

$$\frac{R_1 \cdot A_1}{L_1} = \frac{R_2 \cdot A_2}{L_2}$$

$$\textcircled{R_2} \frac{A_2 L_1}{A_2 L_1} = \frac{R_1 A_1 L_2}{A_2 L_1}$$

$$R_2 = \frac{R_1 A_1 L_2}{A_2 L_1}$$

$$= \frac{0.017 \cdot 1 \cdot 50}{0.25 \cdot 1}$$

$$= 3.4 \Omega$$

Specific Resistance

$$\rho = \frac{RA}{L}$$

$\rho \Rightarrow$ "rho" specific resistance

$R \Rightarrow$ resistance Ω


$A \Rightarrow$ cross sectional area (must be uniform)

$L \Rightarrow$ length

Resistor color code

how to find resistor color code??

Examples:-

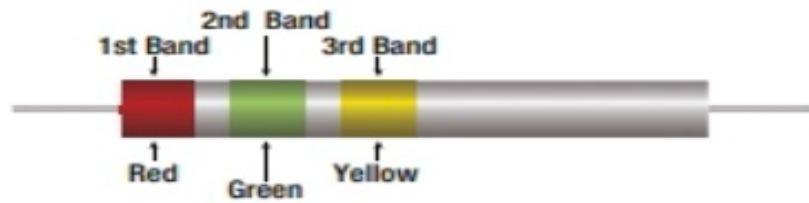

Color	Numerical Value	Significance
1st Band — Red	2	1st Digit
2nd Band — Green	5	2nd Digit
3rd Band — Yellow	4	No. of Zeroes to Add

Figure 7-8. End to center band marking.

Resistor Color Code		
Color	Number	Tolerance
Black	0	—
Brown	1	1%
Red	2	2%
Orange	3	3%
Yellow	4	4%
Green	5	5%
Blue	6	6%
Violet	7	7%
Gray	8	8%
White	9	9%
Gold	—	5%
Silver	—	10%
No color	—	20%

Figure 7-9. Resistor color code.

Note: We must memorize these colors code

first band

second band

add zeros

11 86000 (1)

$$* 86000 \times 0.10 = 8600 \Omega$$

$$* \text{max: } 86000 + 8600 = 94600 \Omega$$

$$* \text{mini: } 86000 - 8600 = 77400 \Omega$$

2 960 (2)

$$* 960 \times 0.05 = 48 \Omega$$

$$* \text{max: } 960 + 48 = 1008 \Omega$$







$$* \text{mini: } 960 - 48 = 912 \Omega$$

3 2500 (3)

$$* 2500 \times 0.02 = 50 \Omega$$

$$* \text{max: } 2500 + 50 = 2550 \Omega$$
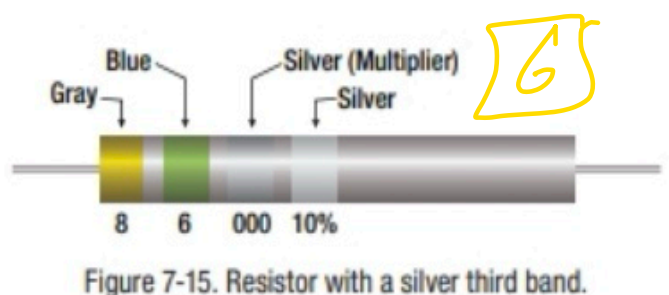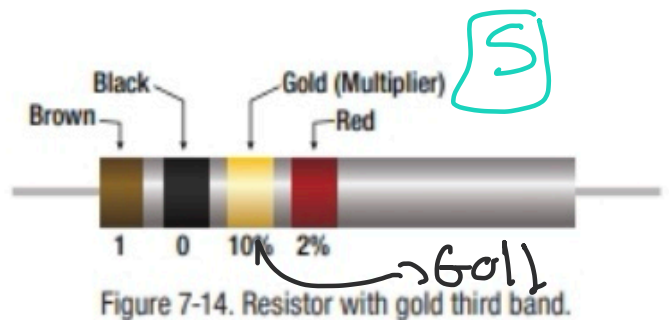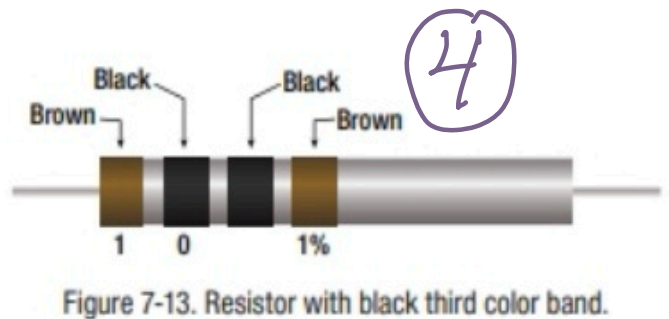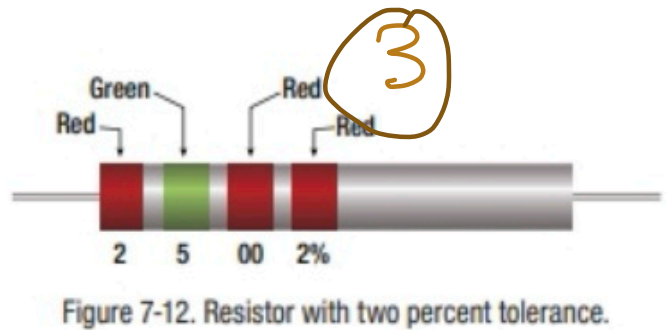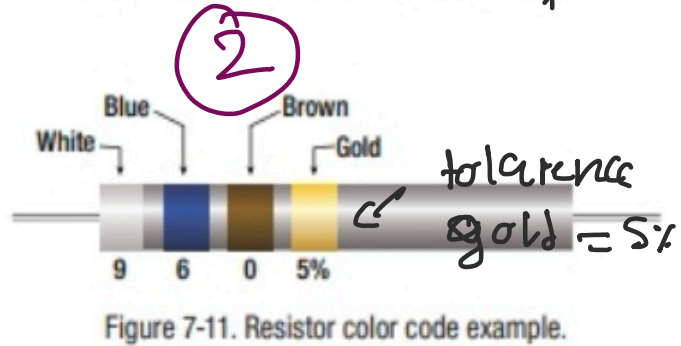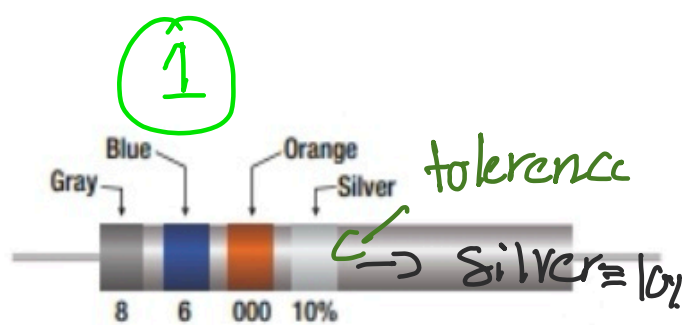
$$* \text{mini: } 2500 - 50 = 2450 \Omega$$



4) 10

4

$$10 \times 0.01 = 0.1 \Omega$$

$$\text{max: } 10 + 0.1 = 10.1 \Omega$$

$$\text{min: } 10 - 0.1 = 9.9 \Omega$$

5) 10

$$10 \times 0.10 = 1$$

$$1 + 0.02 = 1.02$$

$$1 - 0.02 = 0.98$$

6) 86000

6

$$86000 \times 0.10 = 8600$$

$$\text{max: } 86000 + 8600 = 94600 \Omega$$

$$\text{min: } 86000 - 8600 = 77400 \Omega$$

The Resistance in Series / parallel circuit

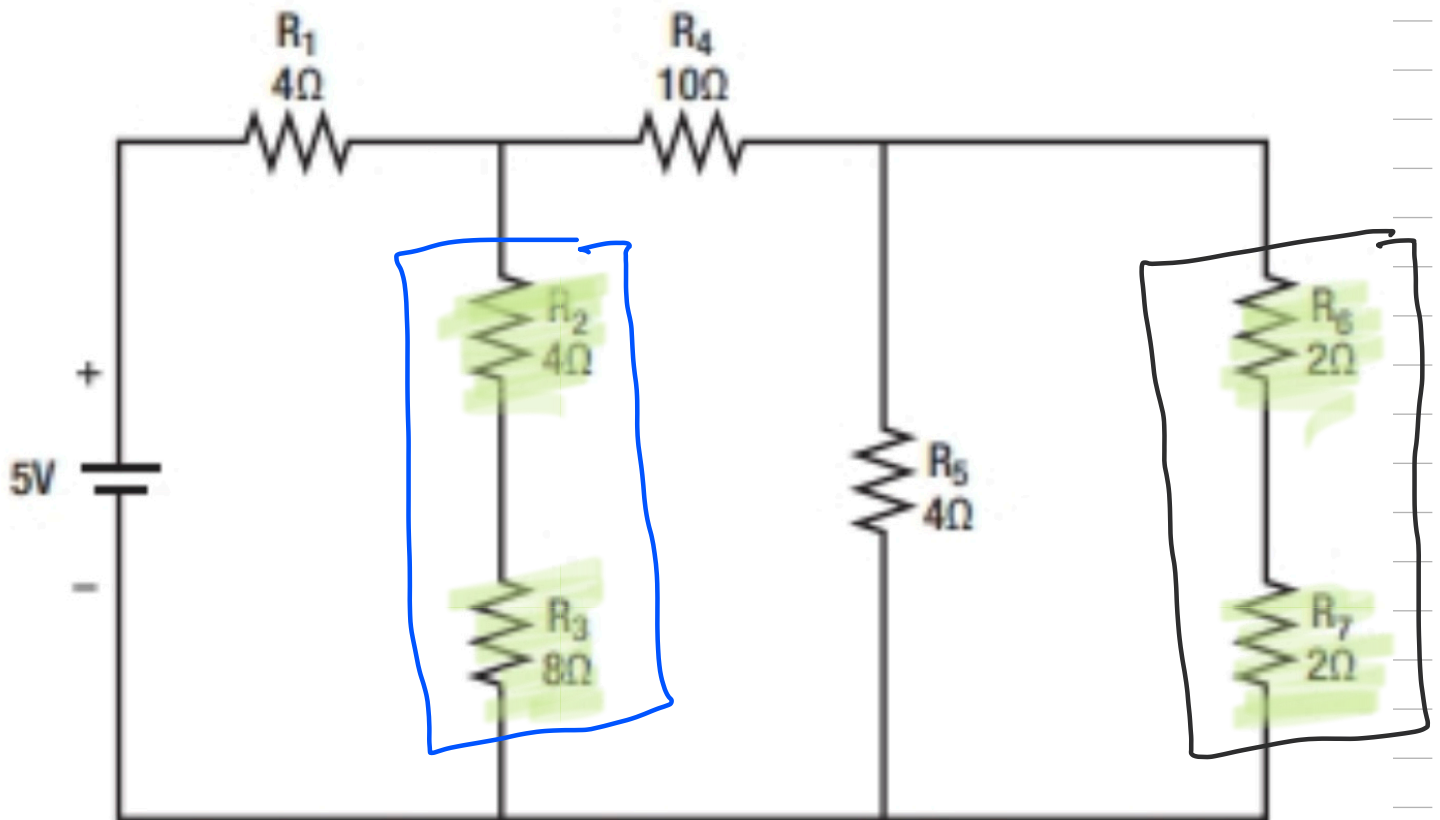


Figure 7-18. Calculations of resistance in circuits containing combinations of series and parallel paths.

[1] $R_2 + R_3$


$$R_{23} = 4 + 8$$

$$R_{23} = 12\Omega$$

[2] $R_6 + R_7$


$$R_{67} = 2 + 2$$

$$R_{67} = 4\Omega$$

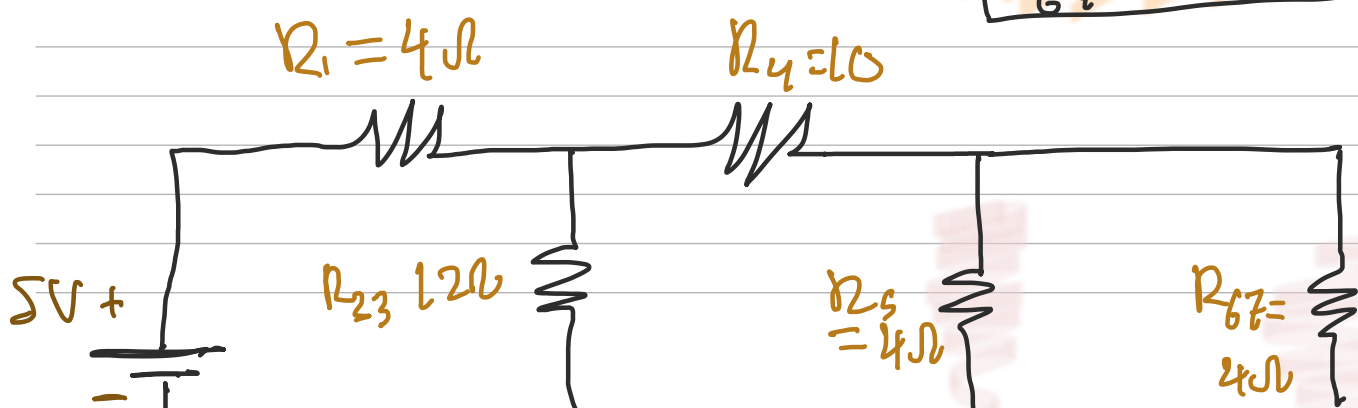

[3] R_5 and R_6 are parallel

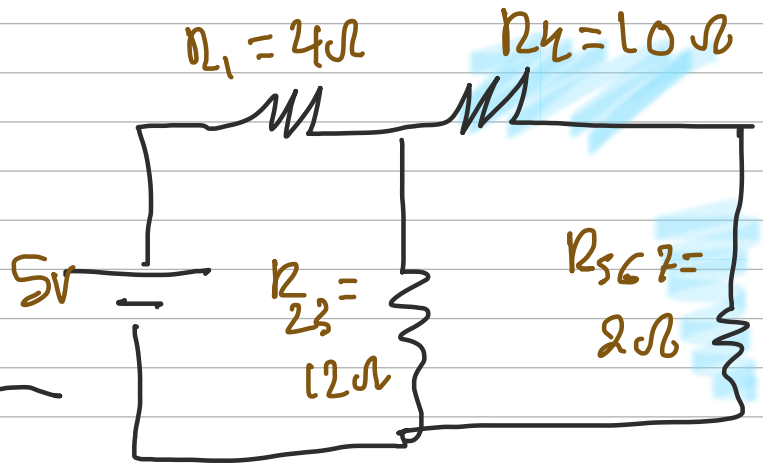
$$R_{567} = \frac{1}{\frac{1}{4} + \frac{1}{4}}$$



$$R_{567} = 2\Omega$$

[4] R_4 and R_{567} are series

$$R_4 + R_{567} = 10 + 2$$

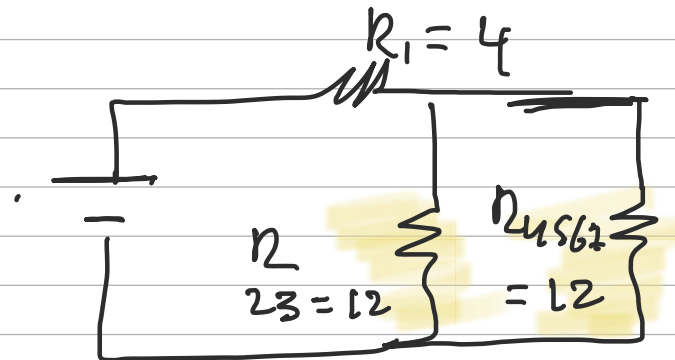

$$R_{4567} = 12\Omega$$

[5] R_{23} and R_{4567} are parallel

$$R_{23 \cup 567} = \frac{1}{\frac{1}{12} + \frac{1}{12}}$$


$$R_{23 \cup 567} = 6\Omega$$

[6] R_1 and R_{234567} are series

$$R_{1234567} = R_1 + R_{234567}$$


$$R_{1234567} = 4 + 6$$

$$R_{1234567} = 10\Omega$$

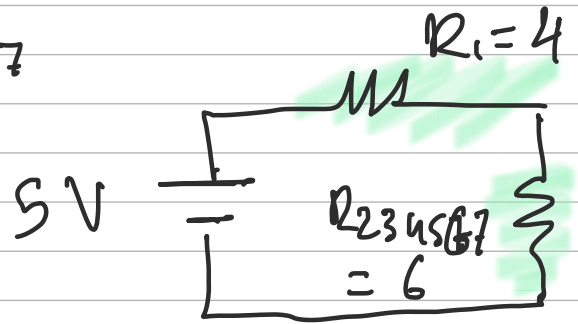

Balanced

= Wheatstone Bridge

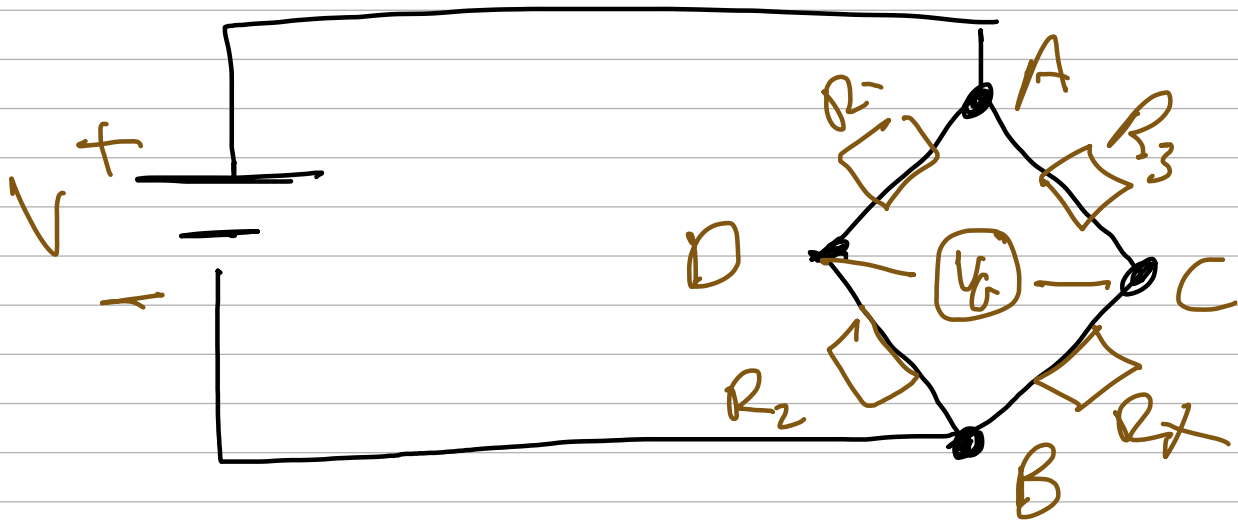

When $V_g = 0$

$$R_1 R_x = R_2 R_3$$


$$R_2 = R_{pot}$$

$$R_1 = R_3$$

$$R_x = R_{pot}$$

Examples:-

$$\frac{30}{60} = \frac{1}{2}$$

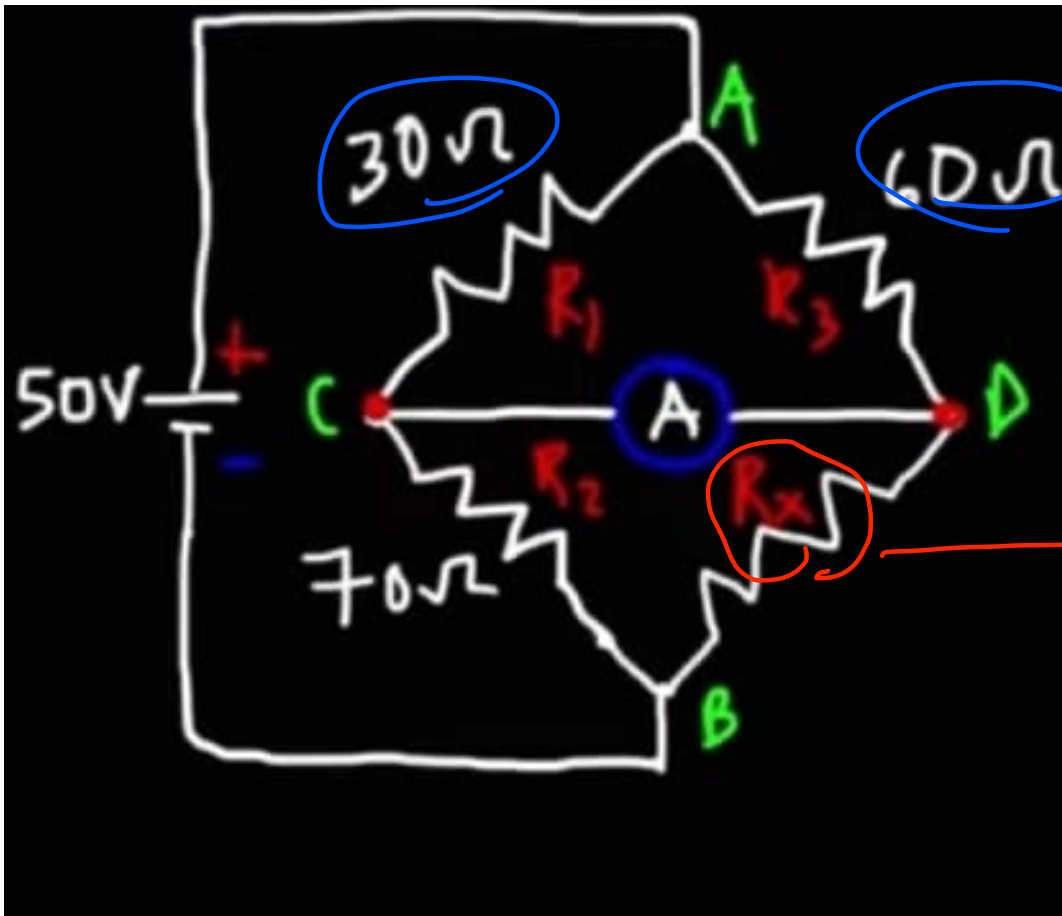

$$\frac{70}{??} = \frac{1}{2}$$

$$70 \times 2 = 140$$

→ unknown

Since R_x
??

$$R_1 R_x = R_2 R_3$$

$$\frac{30}{70} \cdot R_x = \frac{70 \times 60}{30}$$

$$R_x = 140 \Omega$$